
Lab 2

ELECENG 2EJ4

Gurleen Dhillon

dhillg25

400301955

2022-10-10

Part 1

1. (10 points)

- a. Based on the simulation data obtained in Step 1.2, what are the $V_{o,min}$, and I_o of the current sink? Use the measurement data obtained in Step 1.10 to verify the $V_{o,min}$ and I_o .

$V_{o,min}$ in Step 1.2 = -3V

$V_{o,min}$ in Step 1.10 = -3V

I_o in Step 1.2 = 0.000184804mA

I_o in Step 1.10 = 0.0001990623mA

- b. Based on the simulation data obtained in Step 1.2 and the measurement data obtained in Step 1.10, what are the ranges of the simulated and measured output resistance R_o of the current sink for V_{CC} larger than $V_{o,min}$?

Range of R_o for V_{CC} larger than $V_{o,min}$ in Step 1.2 = $[7.50E+7\Omega, 7.69E+7\Omega]$

Range of R_o for V_{CC} larger than $V_{o,min}$ in Step 1.10 = $[-6.97E+6\Omega, 9.54E+5\Omega]$

2. (10 Points) What are the values of V_{o1} and V_{o2} obtained in Step 1.5? Check the Q-points of Q2 under these two conditions and explain/justify the results obtained qualitatively.


V_{o1} in Step 1.5 = 4.94V

V_{o2} in Step 1.5 = -3.58V

Because the value of V_{sig} is outside of the range in V_{O1} and V_{O2} , these values are close to the maximum and minimum output voltages.

3. (15 Points) Based on the simulation data obtained in Step 1.6:

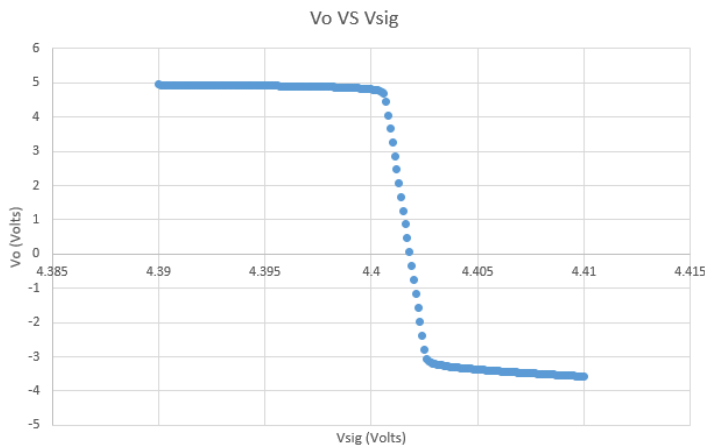- a. plot the simulated DC V_o vs. V_{sig} characteristics. Discuss/justify the simulated characteristics.



This graph is able to tell us when the circuit is able to work as an amplifier within a specific range of volts in V_{sig} and can also tell us the corresponding output voltage for a controlled output voltage in the amplifier.

- b. For the circuit to work as an amplifier, find the DC input range for V_{sig} and the output voltage range for V_o .

Input range for $V_{sig} = [4.4006V, 4.4028V]$


Output voltage for $V_o = [4.675276V, -3.180605V]$

- c. Find the V_{sig} value and its corresponding collector current I_{c2} that results in $V_o \approx 0V$.

$V_{sig} = 4.401799999999997V$

$V_o = 0.05354082V$

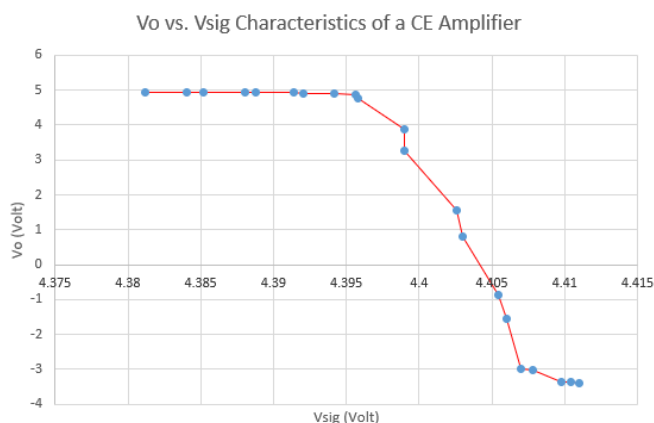- d. Based on the measurement data obtained in Step 1.16, plot the measured DC V_o vs. V_{sig} characteristics.



4. (10 Points)

- a. Based on the simulation data obtained in Step 1.7, what are the magnitude (in dB) and phase of intrinsic voltage gain A_{vo} at low frequency (i.e., 100 Hz) and the upper 3-dB frequency f_{3dB} (i.e., the frequency at which the amplitude become $1/\sqrt{2} = 0.707$ of its low-frequency value, or the phase changes 45°) of this CE amplifier?

The upper 3-dB frequency is about 14077Hz and 135.148 degrees and 2.0269dB.

- b. Verify the voltage gain A_{vo} using the measurement data obtained in Steps 1.18 and 1.19.

- c. Increase the frequency of W1 to the upper 3-dB frequency f_{3dB} obtained from the simulation, check the value of A_{vo} , and see if it is about 0.707 of its low-frequency value obtained at 100 Hz. Provide WaveForms screenshots of your measurement results.

Part 2

5. (15 Points) Based on the simulation data obtained in Step 2.2,

- a. what are the voltages of V_o and V_E , and I_{c2} of Q2 when $V_{CM} = 0V$

$V_o = 4.24999047219929V$

$V_E = -0.5253805V$

$I_{c2} = 0.00009090927A$



- b. what is the input common-mode range (i.e., the voltage range of V_{CM} to maintain the same out voltage), and

Range of V_{cm} where V_o is constant = $[-2.6V, 4.6V]$

- c. what determines the upper and lower bounds of the input common-mode range?

Range is determined at -2.6V and 4.6V. When V_{cm} is higher than this range, V_o gradually increases and when V_{cm} is lower than this range, V_o gradually decreases. Inside the range V_o is stable.

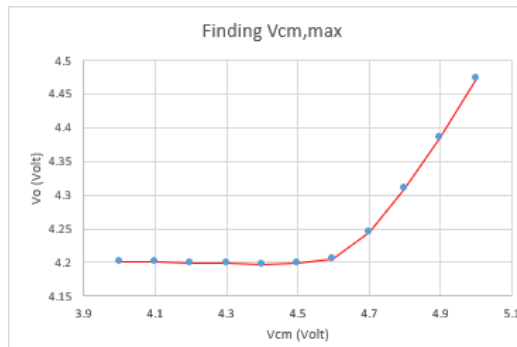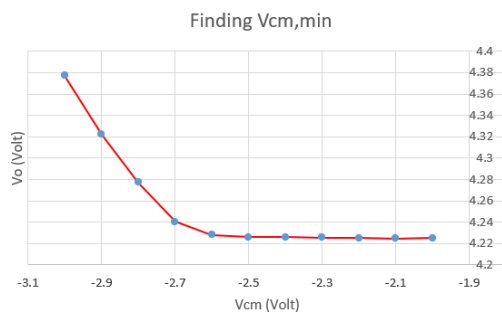- d. Based on the measurement data obtained in Steps 2.7 and 2.8, verify the common-mode range by experimental data.




Based on the graphs in 2.7 and 2.8, we can tell that the $V_{cm,min}$ is between -2.5 and -2.6 and that the $V_{cm,max}$ is between 4.5 and 4.6.

6. (10 Points) Based on the simulated data obtained in Step 2.3, what is the low-frequency voltage gain A_{cm} in dB for the common-mode signal?
Based on the simulated data, the low-frequency voltage gain A_{cm} that was calculated in 2.3 is -86.8dB.

Part 3

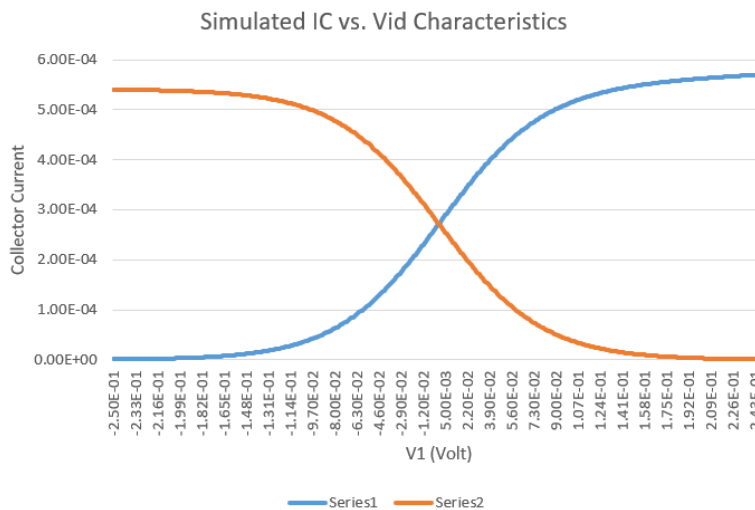7. (10 Points) Based on the simulation data obtained in Step 3.2 and the description in Section 9.2.3 Large-Signal Operation of the textbook,
- what is the input differential-mode range?



The input differential-mode range = $[-0.102V, 0.102V]$.

- How do we determine the upper and lower bounds of the input differential-mode range?

The highest and lowest values occur when the voltage is -0.204V and 0.204V, so to get the upper and lower bounds we simply divide these bounds by 2 to get -0.102V and 0.102V.

8. (10 Points)
- Based on the simulation data obtained in Step 3.3, what is the voltage gain A_d in dB for the differential-mode signal?

Based on the simulated data, the voltage gain A_d that was calculated in 3.3 is 19.63dB.

- Estimate its upper 3-dB frequency f_{3dB} (i.e., the frequency at which the amplitude becomes $1/\sqrt{2} = 0.707$ of its low-frequency value or the phase

changes 45°) and calculate the gain-bandwidth product (GBW) in hertz (Hz).

The upper 3-dB frequency is about 7781962Hz and -44.897 degrees. The gain-bandwidth is 1.34E+08 Hz.

- c. Compare the upper 3-dB frequency f_{3dB} of this differential amplifier with that of the CE amplifier obtained in Q4.

This 3-dB frequency is greater than the value obtained in Q4.

- d. Based on the measurement data obtained in Step 3.6, calculate the measured low-frequency differential voltage gain A_d in dB.

- 9. (10 Points) Based on the simulation data, what is the common-mode rejection ratio (CMRR) of the amplifier in dB?

$$|A_d| / |A_{cm}| = |19.63\text{dB}| / |-86.8\text{dB}| = 0.22615$$